

Octave Keyboard with AutoPlay

Daniel Chen and Vivian Hu

August 26, 2014

The goal of this project was to create a simple one octave keyboard mapped to buttons with the additional capability to autoplay “Kids” by MGMT when a switch is turned on. When the buttons corresponding to notes are pressed, the appropriate notes are played through the speaker, and LEDs which correspond to the keys light up. The LEDs can be disabled using a switch.

This project was created by Vivian Hu and Daniel Chen in Summer 2014 at Dartmouth College for the Digital Electronics (ENGS031/COSC056) course. This report goes over the implementation, design, and usage of the final product, which implements all of these features.

1	Introduction: The Problem	3
2	Design Solution	3
2.1	Specifications	3
2.2	Operating Instructions	4
2.3	Theory of Operation	5
2.4	Construction and Debugging	7
3	Evaluation of Design	7
4	Conclusions and Recommendations	7
5	Acknowledgments	8
5.1	Vivian's Contributions	8
5.2	Daniel's Contributions	8
6	References	9
7	Appendix	10
7.1	System level diagrams	11
7.1.1	Front Panel	11
7.1.2	Block Diagram	11
7.1.3	Schematic Diagram	11
7.1.4	Package Map	12
7.1.5	External Components	12
7.2	Programmed Logic	13
7.2.1	State Diagrams	13
7.2.2	VHDL Code	16
7.2.3	Resource utilization	53
7.2.4	UCF	54
7.3	Memory Map	55
7.4	Timing Diagram	55
7.5	Data Sheets	56

1 Introduction: The Problem

The problem that this project solves is the creation of a one-octave keyboard, and the ability to produce certain sounds through circuit logic. An additional issue is representing the song that will be autoplayed.

2 Design Solution


2.1 Specifications

The inputs to this circuit are:


- 8 Buttons that map to the notes to play (bottom right of image to the right).
- An LED disable switch which disables LED output.
- An AutoPlay switch which enables the playing of “Kids” by MGMT.

The outputs to the circuit are:

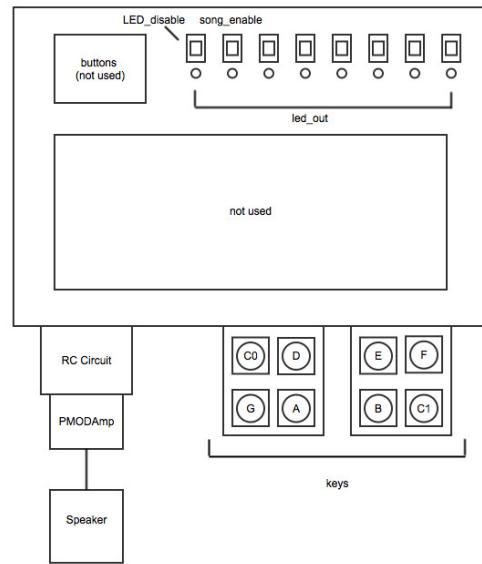- 8 LEDs which correspond to the notes being played.
- A speaker which outputs the notes appropriate to the song or specified by the keys.



The picture shown below displays the datapath and control of the circuit. The controller (a finite state machine) takes in all of the inputs and outputs the LEDs. It emits a signal corresponding to the note that needs to be output (a copy of the LED output) which is the Phase Accumulator receives. The data from the Phase Accumulator transfers to the Sine LUT, which goes to the Pulse Width Modulator... tone

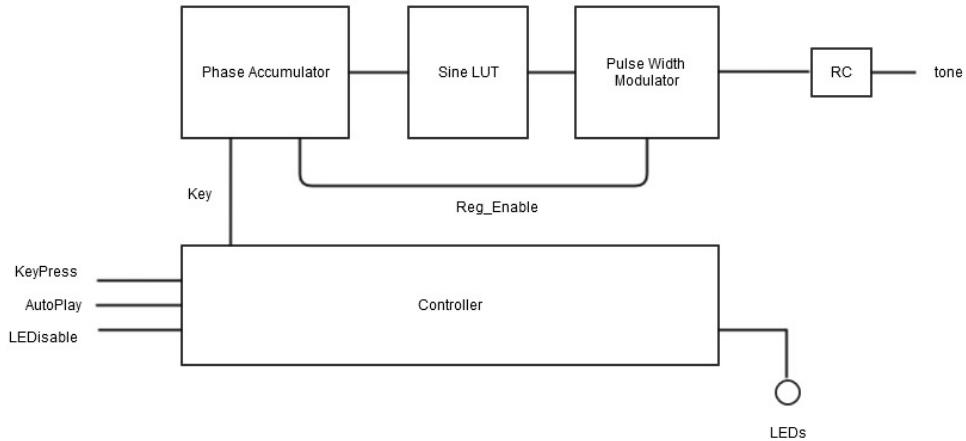

2.2 Operating Instructions

Set up Circuit

To set up the one-octave keyboard circuit, you will need:

- Xilinx ISE Design Suite 14.4
- Digilent Adept
- The source code or the programming file
- 1 x Digilent NEXYS 3 Spartan 6 FPGA
- 2 x 4 button Digilent Button Module
- 1 x Digilent PmodBB
- 1 x Digilent PmodAMP2
- 1 x Speaker

Here are the steps to get the circuit running:

1. (If no bit file) Open the project in Xilinx, generate the programming file.
2. Plug in FPGA (NEXYS 3 Spartan 6) into computer.
3. Insert Digilent Button Modules in the top of JA1 and the top of JB1 on the NEXYS 3.
4. Insert the Digilent PmodBB into JD1.
5. Insert the PmodAMP2 into the top of J4 on the PmodBB.
6. Connect the speaker to J2 on PmodAMP2.
7. Set up the RC circuit on the PmodBB.
8. Open Digilent Adept, select bit file to program the FPGA.

Playing notes

To play notes, press the buttons on the FPGA corresponding to the notes that you want to play. There are two rows of four buttons. The top four buttons represent low c, d, e and f, while the bottom four buttons are g, a, b and high c.

Only one note can be played at a time (first note pressed takes priority), and user-inputted notes only play when the auto-play switch is off.

Auto-play “Kids” by MGMT

To play “Kids” by MGMT, simply flip the AutoPlay switch on. You cannot create additional notes at this time using the buttons.

Disable LEDs

To disable the LEDs that light up corresponding to the notes that are pressed, simply turn on the LED disable switch.

2.3 Theory of Operation

The key component of our keyboard project is the generation of sine waves of varying frequencies using a technique called direct digital synthesis (DDS). To implement this, we use a combination of a phase accumulator and a sine wave lookup table (LUT) to produce wave samples of specific frequencies. In the place of a digital-to-analog converter, we use a pulse width modulator (PWM) to convert these sine wave samples to audio.

The controller of our program is a finite state machine. The controller takes in the user’s input and turns it into a single-note output for the Phase Accumulator and the LEDs. It uses the note that was input first. If two notes are both initially pressed at the same exact time, the lower note is used. When the autoplay switch gets turned on, the state machine moves into hard-coded states that play MGMT’s “Kids.” The song only starts if the user is not currently pressing a key. The song consists of a large number of states that output a time that corresponds to the length of the note or the rest, and waits for either the switch to be turned off (at which point it goes to idle) or for the beat counter to reach its max (at which point it moves to the next note or rest).

The song itself consists of 3 snippets, which repeat in a particular fashion. Given that the three parts are A, B, and C, the song is a repetition of ACACBCBC. To keep track of this, an additional counter is used to determine whether to go to A or B at the end of C. See the appendix for detailed state diagrams related to the controller.

8 different buttons (button module extensions on the FPGA), or “key” serve as the main “playable” interface of the keyboard. In VHDL, the keys are represented as an 8-bit bus input to the controller, where each bit represents a different note. Because our keyboard is monophonic, the controller checks each bit in succession from low to high C and outputs the first note it detects to the FreqLUT. As a result, only one bit in the 8-bit key_out vector received by ToneFreq-LUT should be high at a time; otherwise, when no button is being pressed, all bits are ‘0’. This prevents conflicts when multiple buttons are pressed at once. The

controller also takes in an LED_disable input that disables the LEDs and a song_enable that automatically plays back a pre-programmed song (here “Kids” by MGMT).

Key_out is then used as an index of sorts into the ToneFreq-LUT, which contains the pre-calculated phase increment values for each note, which is related to the desired frequency in the following way where N represents the bit size of the accumulator and fclk is the frequency of the clock. We use N=13 here. This increment value is then passed on to the phase accumulator.

The phase accumulator is essentially an incrementer composed of an adder and a register which increases by the increment value every clock cycle. However, although the system is running at a frequency of about 50MHz in order to reduce noise, in actuality the phase accumulator is updating at a frequency of around 10kHz, at the clk10 signal given by the PWMCounter. As a result, clk10 here serves as an enable. The phase produced by the accumulator is then passed as an input address to the SineLUT. However, because our SineLUT only takes an 8-bit phase, only the 8 most significant bits are used.

To obtain wave samples, this value is then used as an index into a SineLUT supplied by the Xilinx Core Generator. Rather than having to generate all the samples of a waveform everytime, the values of a 2^M (where M is the bit size of our phase) sample wave are simply stored in block memory (BRAM) for easy access. The SineLUT generates a 10-bit sample for conversion by the PWM.

The PWM maps the amplitude of the signal to a square wave pulse by comparing the sample value (which needs to be first converted from two’s complement to unsigned offset binary) to a counter value. When the count is less than the sample, the comparator output is a ‘1’; otherwise the output is a ‘0’. In order to send the clk10 enable to the phase accumulator at a 10kHz frequency, the PWM counter also generates a terminal count signal every 5,000 clock cycles.

The signal then passes through an off-board low-pass RC filter that reduces higher frequency signal noise before passing the tone through to the speaker.

Our circuit also features the additional functionality of automatically playing a pre-programmed song when given the song_enable signal. Most of this work is done by the controller state-machine (ie which note or sequence to go to next). However, in order to get the song to play at an appropriate speed, we implemented an additional BeatCounter that counts at a rate of about 240 beats per minute. When the signal to autoplay the song is given, the controller sends a count_en signal and a number count_to to the beat counter letting it know how long to “hold” the note before sending the terminal tc_tick back to the controller to move on to the next note/state.

2.4 Construction and Debugging

To build the circuit, we began by building and testing the VHDL modules for the PWM. We designed the counter and the comparator and simulated the generation of wave “samples” with a separate counter in the place of our DDS module. In our testbench, we were able to observe the square wave pulses getting wider as the “sample” increased as expected. From there, we implemented the phase accumulator. Testing was simply a matter of assigning an arbitrary number to the increment signal and confirming the values were adding up correctly. The next step was designing a lookup table with phase increment information for each note frequency and mapping it via the top module to the phase accumulator. We did run into a slight problem here with integer arithmetic.

3 Evaluation of Design

Our solution is

4 Conclusions and Recommendations

The original goal of our project was to simply make a one-octave keyboard that plays all the notes in C major. LEDs would light up when notes were played, unless an “LED disable” switch was turned on.

At the end, we were not only able to accomplish our original goal of the simple keyboard but also to add an additional autoplay feature that played “Kids” by MGMT.

For future groups looking to create this project, we would recommend that they really take the time to understand the operation of the circuit before jumping into the project. Another important consideration is to remember to synchronize the inputs and debounce the buttons throughout the project’s creation.

5 Acknowledgments

We would like to thank Eric Hansen and Dave Picard for their support and mentorship throughout not only this project but also the course. We would also like to thank the other students of Digital Electronics as well as the TAs. We'd also like to thank MGMT for an awesome song that conveniently contains itself to a single octave.

5.1 and 5.2 list the contributions for each partner. Although both partners had their hands in most aspects of the project, some components generally had one partner who was more involved in its creation.

5.1 Vivian's Contributions

- Circuit Design
- DDS, PWM, FreqLUT, PlayCount
- RC Circuit
- Block Diagrams

5.2 Daniel's Contributions

- Majority of the controller, including auto-play
- Design and creation of song auto-play, state diagram
- Top level
- Diagrams
- LaTeX for report
- Git creation/management

6 References

- [1] Cordesses, Lionel. "Direct Digital Synthesis: A Tool for Periodic Wave Generation." *IEEE Signal Processing Magazine*. IEEE, July 2004. Web.
- [2] Hansen, Eric. *Lab Assignment 1*. N.p.: ENGS128 - Advanced Digital System Design, Spring 2011. PDF.
- [3] *Introduction to Direct Digital Synthesis*. San Jose: Intel Corporation, June 1991. PDF.
- [4] Palacheria, Amar. *Using PWM to Generate Analog Output*. N.p.: Microchip Technology Inc., 1997. PDF.

7 Appendix

List of Figures

1	Annotated Digital Photo of Project	11
2	Package Map	12
3	State Diagram Defaults	13
4	User Play State Diagram	14
5	Autoplay State Diagram	15
6	OctaveKeyboardTop.vhd	16
7	Controller.vhd	24
8	DDS.vhd	39
9	PWM.vhd	41
10	PlayCount.vhd	44
11	FreqLUT.vhd	46
12	keyboardTB.vhd	49
13	Advanced HDL Synthesis Report	53
14	Device Utilization Summary	53
15	UCF file	54
16	PmodAMP2 Data Sheet Page 1/2	57
17	PmodAMP2 Data Sheet Page 2/2	58
18	PmodBB Schematic	59

List of Tables

1	Parts List	12
---	----------------------	----

7.1 System level diagrams

7.1.1 Front Panel

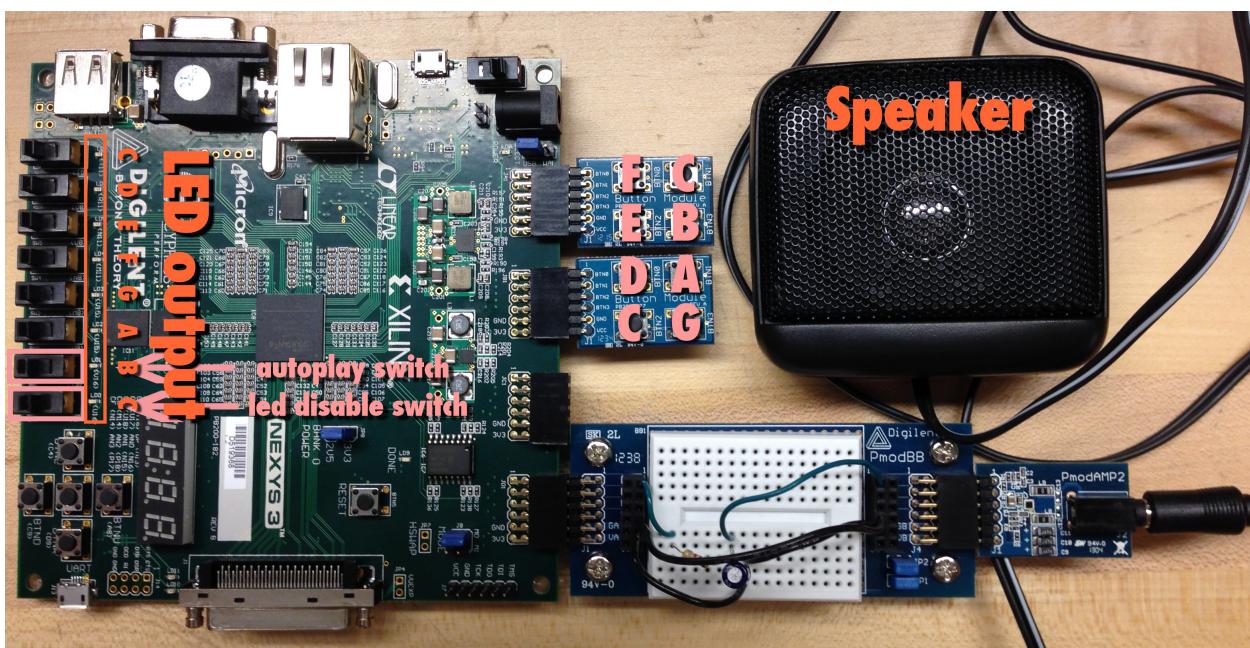


Figure 1: Annotated Digital Photo of Project

7.1.2 Block Diagram

7.1.3 Schematic Diagram

7.1.4 Package Map

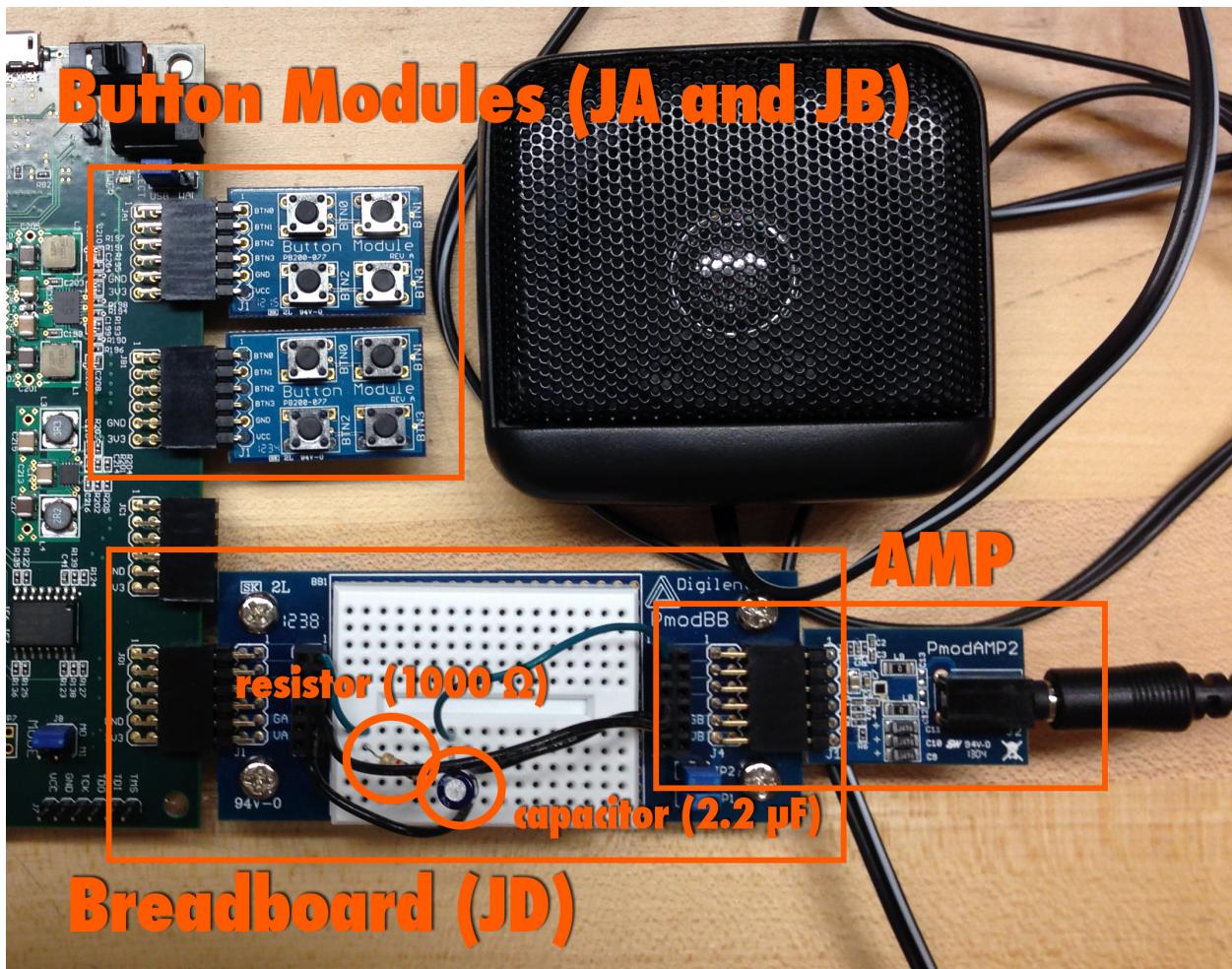


Figure 2: Package Map

7.1.5 External Components

Table 1: Parts List

Reference	Quantity	Description
Nexys3	1	Digilent Nexys3 board
PmodBTN	2	Digilent PmodBTN Push Button. 4 buttons
PmodBB	1	Digilent Bread board
PmodAMP2	1	Digilent Amplifier for monophonic output
Speaker	1	Any generic speaker with standard input

7.2 Programmed Logic

7.2.1 State Diagrams

For simplicity, the state machine for this program is represented in two state diagrams. The first, “User Play State Diagram,” represents the state machine for when the user is given input through the buttons. The second, “Autoplay State Diagram,” represents the state machine when the autoplay mode is on. Both state diagrams share an idle state. If the song enable switch is off, the “User Play State Diagram” should be used. If it is turned on, the “Autoplay State Diagram” should be used.

The program starts at the idle state in the “User Play State Diagram.” If the song enable switch is turned on, the state jumps to autoidle in the “Autoplay State Diagram.” Otherwise, the state changes depending on the user’s input.

Default Values if unspecified:

```
next_state <= curr_state;  
out <= (others => '0');  
key_out <= output;  
count_out <= "0001";  
repeat_tick <= '0';  
beat_en <= '0';
```

Figure 3: State Diagram Defaults

NOTE: If multiple keys are pressed at the exact same time in the idle state, the states are prioritized in terms of lowest to highest notes.

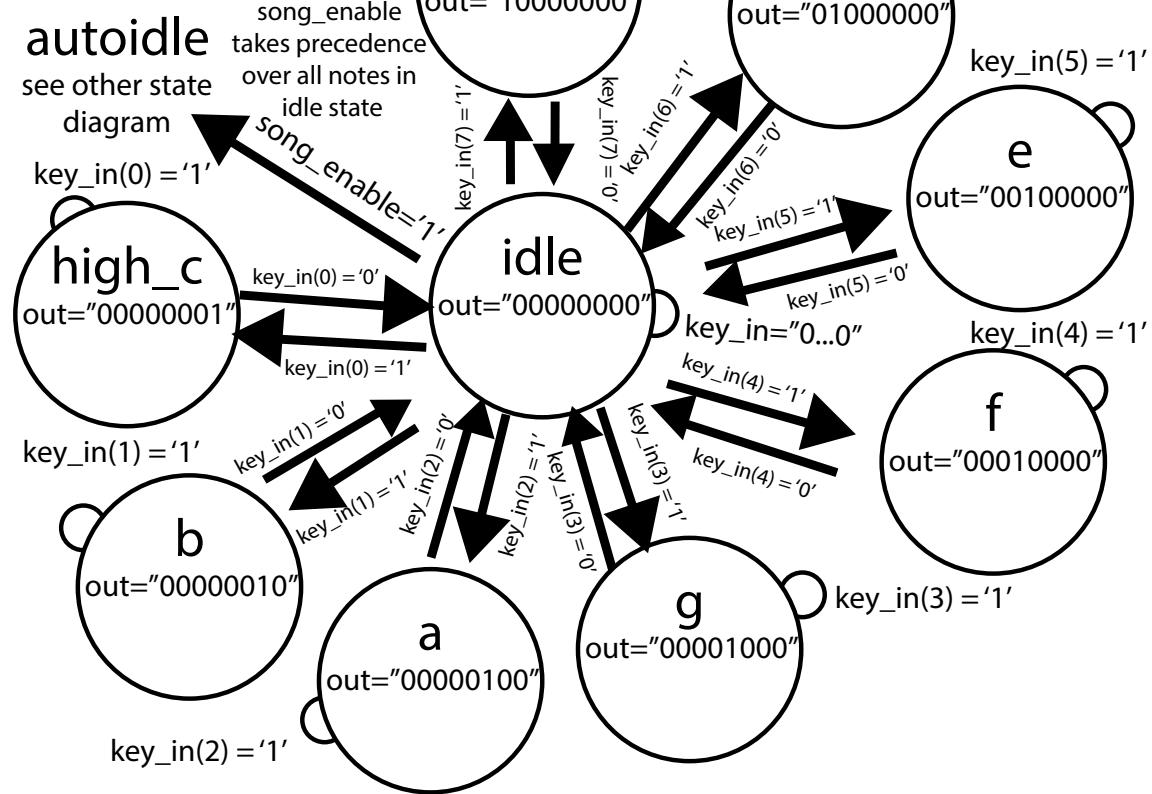


Figure 4: User Play State Diagram

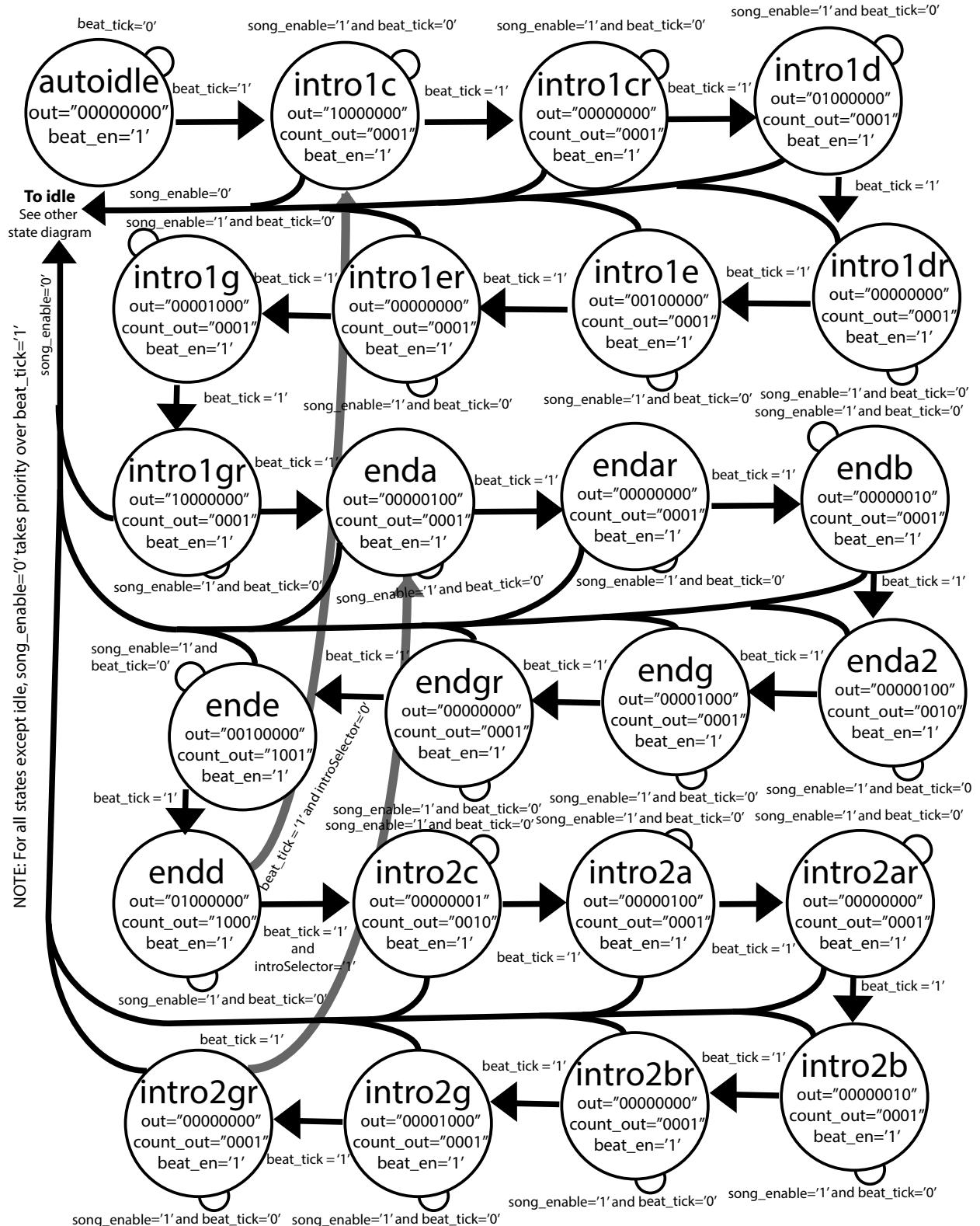


Figure 5: Autoplay State Diagram

7.2.2 VHDL Code

Figure 6: OctaveKeyboardTop.vhd

```
1  -----
2  -- Company: ENGS 31
3  -- Engineer: Vivian Hu, Daniel Chen
4  --
5  -- Create Date: 19:58:26 08/12/2014
6  -- Design Name:
7  -- Module Name: OctaveKeyboardTop - Behavioral
8  -- Project Name: OctaveKeyboard
9  -- Target Devices:
10 -- Tool versions:
11 -- Description: Top level VHDL module for keyboard
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23
24 library UNISIM;
25 use UNISIM.VComponents.all;
26
27 entity OctaveKeyboardTop is
28     Generic (    ACCUMSIZE      : integer := 13;      -- phase accumulator bitsize
```

```

29          INDEXSIZE      : integer := 8;           -- SineLUT index bitsize
30          LUTOUT        : integer := 10);         -- SineLUT out bitsize
31
32  Port ( clk          : in  STD_LOGIC;
33          keys         : in  STD_LOGIC_VECTOR (7 downto 0);
34          led_disable   : in  STD_LOGIC;
35          song_enable   : in  STD_LOGIC;
36          tone          : out STD_LOGIC;
37          shutdown      : out STD_LOGIC;
38          led_out       : out STD_LOGIC_VECTOR (7 downto 0));
39 end OctaveKeyboardTop;
40
41 architecture Behavioral of OctaveKeyboardTop is
42
43     -- signals for 100MHz to 50Mhz clk divider
44     signal clk_en       : std_logic := '0';
45     signal slowclk      : std_logic;
46
47     signal led_disable_sync : std_logic := '0';
48     signal song_enable_sync : std_logic := '0';
49
50     -- mapping signals
51     signal step : std_logic_vector(ACCUMSIZE-1 downto 0) := (others => '0');
52     signal controllerKeys : std_logic_vector(7 downto 0) := (others => '0');
53     signal phase : std_logic_vector(INDEXSIZE-1 downto 0) := (others => '0');
54     signal lutfreq : std_logic_vector(15 downto 0) := (others => '0');
55     signal reg_en : std_logic := '0';
56     signal tempo_en : std_logic := '0';
57     signal keyDB : std_logic_vector(7 downto 0) := (others => '0');
58     signal countDone : std_logic := '0';
59     signal count : std_logic_vector(3 downto 0) := (others => '0');

```

```

61      -- BEGIN component declarations
62
63      COMPONENT Controller
64
65          PORT (    clk           : in      STD_LOGIC;
66                  key_in        : in      STD_LOGIC_VECTOR (7 downto 0);
67                  led_disable   : in      STD_LOGIC;
68                  song_enable   : in      STD_LOGIC;
69                  beat_tick     : in      STD_LOGIC;
70                  beat_en       : out     STD_LOGIC;
71                  count_out     : out     STD_LOGIC_VECTOR(3 downto 0);
72                  key_out       : out     STD_LOGIC_VECTOR (7 downto 0);
73                  led_out       : out     STD_LOGIC_VECTOR (7 downto 0));
74
75      END COMPONENT;
76
77
78      COMPONENT FreqLUT
79
80          PORT (    clk           : in      STD_LOGIC;
81                  key_in        : in      STD_LOGIC_VECTOR (7 downto 0);
82                  increment     : out     STD_LOGIC_VECTOR (ACCUMSIZE-1 downto 0));
83
84      END COMPONENT;
85
86
87      COMPONENT DDS
88
89          PORT (    clk           : in      STD_LOGIC;
90                  clk10         : in      STD_LOGIC;
91                  step          : in      STD_LOGIC_VECTOR(ACCUMSIZE-1 downto 0);
92                  phase         : out     STD_LOGIC_VECTOR(INDEXSIZE-1 downto 0));
93
94      END COMPONENT;
95
96
97      COMPONENT PWM
98
99          PORT (    clk           : in      STD_LOGIC;
100                  sample        : in      STD_LOGIC_VECTOR(LUTOUT-1 downto 0);
101                  slowclk       : out     STD_LOGIC;
102 );

```



```

122         led_disable_sync <= led_disable;
123         song_enable_sync <= song_enable;
124     end if;
125 end process SynchronizeSwitches;
126
127 -- slow main clock down by half (here: 100Mhz to 50Mhz)
128 clkDivider: process(clk)
129 begin
130     if rising_edge(clk) then
131         clk_en <= NOT(clk_en);
132     end if;
133 end process clkDivider;
134
135 -- map signals
136 shutdown <= '1';           -- tie shutdown signal high for speaker pmod
137
138 slowclk_buf: BUFG
139     Port map ( I => clk_en,
140                 0 => slowclk );
141
142
143 debouncer0: debounce
144     Port map ( clk => slowclk,
145                 switch => keys(0),
146                 dbswitch => keyDB(0) );
147
148 debouncer1: debounce
149     Port map ( clk => slowclk,
150                 switch => keys(1),
151                 dbswitch => keyDB(1) );
152

```

```

153      debouncer2: debounce
154          Port map (  clk => slowclk,
155                      switch => keys(2),
156                      dbswitch => keyDB(2) );
157
158      debouncer3: debounce
159          Port map (  clk => slowclk,
160                      switch => keys(3),
161                      dbswitch => keyDB(3) );
162
163      debouncer4: debounce
164          Port map (  clk => slowclk,
165                      switch => keys(4),
166                      dbswitch => keyDB(4) );
167
168      debouncer5: debounce
169          Port map (  clk => slowclk,
170                      switch => keys(5),
171                      dbswitch => keyDB(5) );
172
173      debouncer6: debounce
174          Port map (  clk => slowclk,
175                      switch => keys(6),
176                      dbswitch => keyDB(6) );
177
178      debouncer7: debounce
179          Port map (  clk => slowclk,
180                      switch => keys(7),
181                      dbswitch => keyDB(7) );
182
183      KeyControl: Controller

```

```

184      PORT MAP (  clk          => slowclk,
185                  key_in       => keyDB,
186                  led_disable  => led_disable_sync,
187                  song_enable  => song_enable_sync,
188                  beat_tick    => countdone,
189                  beat_en      => tempo_en,
190                  count_out    => count,
191                  key_out      => controllerKeys,
192                  led_out       => led_out);
193
194  KeyFrequencies: FreqLUT
195      PORT MAP (  clk          => slowclk,
196                  key_in       => controllerKeys,
197                  increment   => step);
198
199  PhaseAccum: DDS
200      PORT MAP (  clk          => slowclk,
201                  clk10        => reg_en,
202                  step         => step,
203                  phase        => phase);
204
205  PulseWM: PWM
206      PORT MAP (  clk          => slowclk,
207                  sample       => lutfreq(9 downto 0),
208                  slowclk     => reg_en,
209                  pulse        => tone);
210
211  SinFreqs: SinLUT
212      PORT MAP (  aclk         => slowclk,
213                  s_axis_phase_tvalid => '1',
214                  s_axis_phase_tdata   => phase,
```

```
215             m_axis_data_tvalid      => open,
216             m_axis_data_tdata       => lutfreq);
217
218     kidsCounter: PlayCount
219         PORT MAP      ( clk => slowclk,
220                           count_en => tempo_en,
221                           count_to => count,
222                           tc_tick => countDone);
223
224 end Behavioral;
```

Figure 7: Controller.vhd

```
1  --
2  -- Company: ENGS041 14X
3  -- Engineer: Vivian Hu and Daniel Chen
4  --
5  -- Create Date:    14:49:26 08/11/2014
6  -- Design Name: Controller FSM
7  -- Module Name:   Controller - Behavioral
8  -- Project Name: Octave Keyboard
9  -- Target Devices: Spartan 6
10 -- Tool versions:
11 -- Description: Basic controller which converts to monotone.
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 --
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23
24 entity Controller is
25     Port (      clk          : in  STD_LOGIC;
26             key_in       : in  STD_LOGIC_VECTOR(7 downto 0);
27             led_disable : in  STD_LOGIC;
28             song_enable : in  STD_LOGIC;
29             beat_tick   : in  STD_LOGIC;
```

```

30         beat_en      : out STD_LOGIC;
31         count_out    : out STD_LOGIC_VECTOR(3 downto 0);
32         key_out      : out STD_LOGIC_VECTOR(7 downto 0);
33         led_out       : out STD_LOGIC_VECTOR(7 downto 0));
34     end Controller;
35
36     architecture Behavioral of Controller is
37         type statetype is (idle, low_c, d, e, f, g, a, b, high_c, autoidle,
38                             intro1c, intro1cr, intro1d, intro1dr, intro1e, intro1er, intro1g, intro1gr,
39                             enda, endar, endb, enda2, endg, endgr, ende, endd,
40                             intro2c, intro2a, intro2ar, intro2b, intro2br, intro2g, intro2gr
41                             );
42         signal curr_state, next_state : statetype := idle;
43         signal output : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
44         signal reps : STD_LOGIC := '1';
45         signal introSelector : STD_LOGIC := '0';
46         signal repeat_tick : STD_LOGIC := '0';
47     begin
48
49         StateUpdate: process(clk)
50     begin
51             if rising_edge(clk) then
52                 curr_state <= next_state;
53             end if;
54         end process StateUpdate;
55
56         CombLogic: process(curr_state, next_state, key_in, led_disable, output,
57                             beat_tick, song_enable, introSelector)
58     begin
59         -- defaults
60         next_state <= curr_state;

```

```

61         output <= (others => '0');
62
63         key_out <= output;
64
65         count_out <= "0001";
66
67         repeat_tick <= '0';
68
69         beat_en <= '0';
70
71
72
73         if (led_disable = '1') then
74
75             led_out <= (others => '0');
76
77         else
78
79             led_out <= output;
80
81         end if;
82
83
84         case curr_state is
85
86             when idle =>
87
88                 if song_enable = '1' then
89
90                     next_state <= autoidle;
91
92                 elsif key_in(7) = '1' then
93
94                     next_state <= low_c;
95
96                 elsif key_in(6) = '1' then
97
98                     next_state <= d;
99
100                elsif key_in(5) = '1' then
101
102                    next_state <= e;
103
104                elsif key_in(4) = '1' then
105
106                    next_state <= f;
107
108                elsif key_in(3) = '1' then
109
110                    next_state <= g;
111
112                elsif key_in(2) = '1' then
113
114                    next_state <= a;
115
116                elsif key_in(1) = '1' then
117
118
```

```

92         next_state <= b;
93
94     elsif key_in(0) = '1' then
95         next_state <= high_c;
96
97     else
98
99         next_state <= idle;
100
101    end if;
102
103
104
105    when low_c =>
106
107        output <= "10000000";
108
109    if key_in(7) = '0' then
110        next_state <= idle;
111
112    end if;
113
114
115    when d =>
116
117        output <= "01000000";
118
119    if key_in(6) = '0' then
120        next_state <= idle;
121
122    end if;
123
124
125    when e =>
126
127        output <= "00100000";
128
129    if key_in(5) = '0' then
130        next_state <= idle;
131
132    end if;
133
134
135    when f =>
136
137        output <= "00010000";
138
139    if key_in(4) = '0' then
140        next_state <= idle;
141
142    end if;
143
144
145
```

```

123      when g =>
124          output <= "00001000";
125          if key_in(3) = '0' then
126              next_state <= idle;
127          end if;
128
129      when a =>
130          output <= "00000100";
131          if key_in(2) = '0' then
132              next_state <= idle;
133          end if;
134
135      when b =>
136          output <= "00000010";
137          if key_in(1) = '0' then
138              next_state <= idle;
139          end if;
140
141      when high_c =>
142          output <= "00000001";
143          if key_in(0) = '0' then
144              next_state <= idle;
145          end if;
146
147      when autoidle =>
148          beat_en <= '1';
149          output <= (others => '0');
150          if (beat_tick = '1') then
151              next_state <= intro1c;
152          end if;
153

```

```

154      when intro1c =>
155          beat_en <= '1';
156          output <= "10000000";
157          count_out <= "0001";
158          if (song_enable = '0') then
159              next_state <= idle;
160          elsif(beat_tick = '1') then
161              next_state <= intro1cr;
162          end if;
163
164
165      when intro1cr =>
166          beat_en <= '1';
167          output <= "00000000";
168          count_out <= "0001";
169          if (song_enable = '0') then
170              next_state <= idle;
171          elsif(beat_tick = '1') then
172              next_state <= intro1d;
173          end if;
174
175
176      when intro1d =>
177          beat_en <= '1';
178          output <= "01000000";
179          count_out <= "0001";
180          if (song_enable = '0') then
181              next_state <= idle;
182          elsif(beat_tick = '1') then
183              next_state <= intro1dr;
184          end if;

```

```

185
186
187     when intro1dr =>
188         beat_en <= '1';
189         output <= "00000000";
190         count_out <= "0001";
191         if (song_enable = '0') then
192             next_state <= idle;
193         elsif(beat_tick = '1') then
194             next_state <= intro1e;
195         end if;
196
197
198     when intro1e =>
199         beat_en <= '1';
200         output <= "00100000";
201         count_out <= "0001";
202         if (song_enable = '0') then
203             next_state <= idle;
204         elsif(beat_tick = '1') then
205             next_state <= intro1er;
206         end if;
207
208
209     when intro1er =>
210         beat_en <= '1';
211         output <= "00000000";
212         count_out <= "0001";
213         if (song_enable = '0') then
214             next_state <= idle;
215         elsif(beat_tick = '1') then

```

```

216         next_state <= intro1g;
217
218
219
220     when intro1g =>
221
222         beat_en <= '1';
223
224         output <= "00001000";
225
226         count_out <= "0001";
227
228         if (song_enable = '0') then
229
230             next_state <= idle;
231
232         elsif(beat_tick = '1') then
233
234             next_state <= intro1gr;
235
236         end if;
237
238
239
240
241
242     when intro1gr =>
243
244         beat_en <= '1';
245
246         output <= "00000000";
247
248         count_out <= "0001";
249
250         if (song_enable = '0') then
251
252             next_state <= idle;
253
254         elsif(beat_tick = '1') then
255
256             next_state <= enda;
257
258         end if;
259
260
261
262     when enda =>
263
264         beat_en <= '1';
265
266         output <= "00000100";
267
268         count_out <= "0001";
269
270         if (song_enable = '0') then

```

```

247         next_state <= idle;
248
249         elsif(beat_tick = '1') then
250             next_state <= endar;
251
252
253     when endar =>
254
255         beat_en <= '1';
256
257         output <= "00000000";
258
259         count_out <= "0001";
260
261         if (song_enable = '0') then
262             next_state <= idle;
263
264         elsif(beat_tick = '1') then
265             next_state <= endb;
266
267         end if;
268
269
270     when endb =>
271
272         beat_en <= '1';
273
274         output <= "00000010";
275
276         count_out <= "0001";
277
278         if (song_enable = '0') then
279             next_state <= idle;
280
281         elsif(beat_tick = '1') then
282             next_state <= enda2;
283
284         end if;
285
286
287     when enda2 =>
288
289         beat_en <= '1';
290
291         output <= "00000100";

```

```

278         count_out <= "0010";
279
280         if (song_enable = '0') then
281             next_state <= idle;
282
283         elsif(beat_tick = '1') then
284             next_state <= endg;
285
286         end if;
287
288
289
290         when endg =>
291             beat_en <= '1';
292             output <= "00001000";
293             count_out <= "0001";
294
295             if (song_enable = '0') then
296                 next_state <= idle;
297
298             elsif(beat_tick = '1') then
299                 next_state <= endgr;
300
301             end if;
302
303
304         when endgr =>
305             beat_en <= '1';
306             output <= "00000000";
307             count_out <= "0001";
308
309             if (song_enable = '0') then
310                 next_state <= idle;
311
312             elsif(beat_tick = '1') then
313                 next_state <= ende;
314
315             end if;
316
317
318         when ende =>

```

```

309         beat_en <= '1';
310
311         output <= "00100000";
312
313         count_out <= "1001";
314
315         if (song_enable = '0') then
316
317             next_state <= idle;
318
319             elsif(beat_tick = '1') then
320
321                 next_state <= endd;
322
323             end if;
324
325
326
327             when endd =>
328
329                 beat_en <= '1';
330
331                 output <= "01000000";
332
333                 count_out <= "1000";
334
335
336                 if (beat_tick = '1') then
337
338                     repeat_tick <= '1';
339
340
341                     if (introSelector = '0') then
342
343                         next_state <= intro1c;
344
345                     else
346
347                         next_state <= intro2c;
348
349                     end if;
350
351
352
353                     elsif (song_enable = '0') then
354
355                         next_state <= idle;
356
357
358                     end if;
359
360
361             when intro2c =>
362
363                 beat_en <= '1';

```

```

340         output <= "00000001";
341
342         count_out <= "0010";
343
344         if (song_enable = '0') then
345
346             next_state <= idle;
347
348
349         elsif(beat_tick = '1') then
350
351             next_state <= intro2a;
352
353         end if;
354
355
356
357         when intro2a =>
358
359             beat_en <= '1';
360
361             output <= "00000100";
362
363             count_out <= "0001";
364
365             if (song_enable = '0') then
366
367                 next_state <= idle;
368
369             elsif(beat_tick = '1') then
370
371                 next_state <= intro2ar;
372
373             end if;
374
375
376
377         when intro2ar =>
378
379             beat_en <= '1';
380
381             output <= "00000000";
382
383             count_out <= "0001";
384
385             if (song_enable = '0') then
386
387                 next_state <= idle;
388
389             elsif(beat_tick = '1') then
390
391                 next_state <= intro2b;
392
393             end if;
394
395
396
779
779

```

```

371      when intro2b =>
372          beat_en <= '1';
373          output <= "00000010";
374          count_out <= "0001";
375          if (song_enable = '0') then
376              next_state <= idle;
377          elsif(beat_tick = '1') then
378              next_state <= intro2br;
379          end if;
380
381
382      when intro2br =>
383          beat_en <= '1';
384          output <= "00000000";
385          count_out <= "0001";
386          if (song_enable = '0') then
387              next_state <= idle;
388          elsif(beat_tick = '1') then
389              next_state <= intro2g;
390          end if;
391
392
393      when intro2g =>
394          beat_en <= '1';
395          output <= "00001000";
396          count_out <= "0001";
397          if (song_enable = '0') then
398              next_state <= idle;
399          elsif(beat_tick = '1') then
400              next_state <= intro2gr;
401          end if;

```

```

402
403
404     when intro2gr =>
405         beat_en <= '1';
406         output <= "00000000";
407         count_out <= "0001";
408         if (song_enable = '0') then
409             next_state <= idle;
410         elsif(beat_tick = '1') then
411             next_state <= enda;
412         end if;
413
414     when others =>
415         next_state <= idle;
416
417     end case;
418
419 end process CombLogic;
420
421 RepeatCounter: process(clk, repeat_tick, reps, introselector)
422 begin
423     if (rising_edge(clk)) then
424         if (repeat_tick = '1') then
425             if (reps = '1') then
426                 introSelector <= not introSelector;
427                 reps <= '0';
428             else
429                 reps <= not reps;
430             end if;
431         end if;
432     end if;

```

```
433      end process RepeatCounter;
```

```
434
```

```
435  end Behavioral;
```

Figure 8: DDS.vhd

```
1  -----
2  -- Company: ENGS031 14X
3  -- Engineer: Vivian Hu and Daniel Chen
4  --
5  -- Create Date: 14:29:30 08/11/2014
6  -- Design Name: Octave Keyboard
7  -- Module Name: DDS - Behavioral
8  -- Project Name: Octave Keyboard
9  -- Target Devices: Spartan 6
10 -- Tool versions:
11 -- Description: Direct Digital Synthesis
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23
24 entity DDS is
25     Generic ( ACCUMSIZE : integer := 13;
26               INDEXSIZE : integer := 8;
27               CLKFREQ   : integer := 100000000);
28
29     Port ( clk      : in STD_LOGIC;
```

```

30      step    : in  STD_LOGIC_VECTOR(ACCUMSIZE-1 downto 0);
31      clk10   : in  STD_LOGIC;
32      phase   : out STD_LOGIC_VECTOR(INDEXSIZE-1 downto 0));
33  end DDS;
34
35 architecture Behavioral of DDS is
36     signal curr_phase : unsigned(ACCUMSIZE-1 downto 0) := (others => '0');
37 begin
38     AccumPhase: process(clk, clk10)
39     begin
40         if (rising_edge(clk)) then
41             if (clk10 = '1') then
42                 curr_phase <= curr_phase + unsigned(step);
43             end if;
44         end if;
45     end process AccumPhase;
46
47     phase <= std_logic_vector(curr_phase(ACCUMSIZE-1 downto ACCUMSIZE-INDEXSIZE));
48 end Behavioral;

```

Figure 9: PWM.vhd

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    10:13:11 08/13/2014
6  -- Design Name:
7  -- Module Name:   PWM - Behavioral
8  -- Project Name:
9  -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23
24 entity PWM is
25     Generic ( LUTOUT      : integer := 10;
26               CLKFREQ      : integer := 100000000);
27
28     Port ( clk : in STD_LOGIC;
29            sample : in STD_LOGIC_VECTOR(LUTOUT-1 downto 0);
```

```

30         slowclk : out STD_LOGIC;
31
32     end PWM;
33
34 architecture Behavioral of PWM is
35
36     signal count : unsigned(13 downto 0) := (others => '0');
37
38 begin
39
40     PWM: process(clk, sample)
41
42         begin
43             -- SinLUT output from two's complement to unsigned offset binary
44             offset <= unsigned(not sample(LUTOUT-1) & sample(LUTOUT-2 downto 0));
45
46             if (rising_edge(clk)) then
47
48                 -- counter running at 50Mhz, but register updating at 10khz
49                 count <= count + 1;
50
51             if (count(9 downto 0) < offset) then
52
53                 pulse <= '1';
54
55             else
56
57                 pulse <= '0';
58
59             end if;
60
61             if (count = max) then
62
63                 slowclk <= '1';
64
65                 count <= (others => '0');
66
67             else
68
69                 slowclk <= '0';
70
71             end if;
72
73         end process;
74
75     end Behavioral;

```

```
61         end if;  
62     end if;  
63 end process PWM;  
64 end Behavioral;
```

Figure 10: PlayCount.vhd

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    11:40:24 08/16/2014
6  -- Design Name:
7  -- Module Name:   PlayCount - Behavioral
8  -- Project Name:
9  -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23
24 entity PlayCount is
25     Port ( clk : in STD_LOGIC;
26             count_en : in STD_LOGIC;
27             count_to : in STD_LOGIC_VECTOR (3 downto 0);
28             tc_tick : out STD_LOGIC);
29 end PlayCount;
30
```

```

31  architecture Behavioral of PlayCount is
32      constant QRTR_CLK_DIV      : integer := 12500000;
33      signal    clkcount      : integer := 0;
34      signal    count         : unsigned(3 downto 0) := "0001";
35  begin
36
37      Qrtr_Sec_Count: process(clk)
38          begin
39              if (rising_edge(clk)) then
40
41                  if (count_en = '1') then
42                      tc_tick <= '0';
43
44                  if (clkcount = QRTR_CLK_DIV - 1) then
45                      if (count = unsigned(count_to)) then
46                          tc_tick <= '1';
47                          count <= "0001";
48                      else
49                          count <= count + 1;
50                      end if;
51
52                      clkcount <= 0;
53                  else
54                      clkcount <= clkcount + 1;
55                  end if;
56              else
57                  tc_tick <= '0';
58              end if;
59          end if;
60      end process Qrtr_Sec_Count;
61  end Behavioral;

```

Figure 11: FreqLUT.vhd

```
1  --
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:      15:30:42 08/11/2014
6  -- Design Name:
7  -- Module Name:     FreqLUT - Behavioral
8  -- Project Name:
9  -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 --
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23
24 entity FreqLUT is
25     Generic ( ACCUMSIZE : integer := 13;
26               CLKFREQ    : integer := 10000);
27
28     Port ( clk : in STD_LOGIC;
29            key_in : in STD_LOGIC_VECTOR (7 downto 0);
```

```

30      increment : out STD_LOGIC_VECTOR (ACCUMSIZE-1 downto 0));
31  end FreqLUT;
32
33 architecture Behavioral of FreqLUT is
34     constant PHASECONSTANT : integer := 2**ACCUMSIZE;
35     constant LOWC : integer := 262;
36     constant D : integer := 294;
37     constant E : integer := 330;
38     constant F : integer := 349;
39     constant G : integer := 392;
40     constant A : integer := 440;
41     constant B : integer := 494;
42     constant HIGHC : integer := 523;
43 begin
44
45     getIncrement: process(key_in)
46     begin
47
48         if (key_in(7) = '1') then
49             increment <= std_logic_vector(to_unsigned(LOWC * PHASECONSTANT / CLKFREQ, ACCUMSIZE));
50         elsif (key_in(6) = '1') then
51             increment <= std_logic_vector(to_unsigned(D * PHASECONSTANT / CLKFREQ, ACCUMSIZE));
52         elsif (key_in(5) = '1') then
53             increment <= std_logic_vector(to_unsigned(E * PHASECONSTANT / CLKFREQ, ACCUMSIZE));
54         elsif (key_in(4) = '1') then
55             increment <= std_logic_vector(to_unsigned(F * PHASECONSTANT / CLKFREQ, ACCUMSIZE));
56         elsif (key_in(3) = '1') then
57             increment <= std_logic_vector(to_unsigned(G * PHASECONSTANT / CLKFREQ, ACCUMSIZE));
58         elsif (key_in(2) = '1') then
59             increment <= std_logic_vector(to_unsigned(A * PHASECONSTANT / CLKFREQ, ACCUMSIZE));
60         elsif (key_in(1) = '1') then

```

```
61      increment <= std_logic_vector(to_unsigned(B * PHASECONSTANT / CLKFREQ, ACCUMSIZE));  
62  
63      elsif (key_in(0) = '1') then  
64          increment <= std_logic_vector(to_unsigned(HIGHC * PHASECONSTANT / CLKFREQ, ACCUMSIZE));  
65      else  
66          increment <= (others => '0');  
67      end if;  
68  
69  
70  end Behavioral;
```

Figure 12: keyboardTB.vhd

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date: 15:16:28 08/17/2014
6  -- Design Name:
7  -- Module Name: C:/Users/F000JW7/Desktop/octave-keyboard/OctaveKeyboard/KeyboardTB.vhd
8  -- Project Name: OctaveKeyboard
9  -- Target Device:
10 -- Tool versions:
11 -- Description:
12 --
13 -- VHDL Test Bench Created by ISE for module: OctaveKeyboardTop
14 --
15 -- Dependencies:
16 --
17 -- Revision:
18 -- Revision 0.01 - File Created
19 -- Additional Comments:
20 --
21 -- Notes:
22 -- This testbench has been automatically generated using types std_logic and
23 -- std_logic_vector for the ports of the unit under test. Xilinx recommends
24 -- that these types always be used for the top-level I/O of a design in order
25 -- to guarantee that the testbench will bind correctly to the post-implementation
26 -- simulation model.
27 -----
28 LIBRARY ieee;
29 USE ieee.std_logic_1164.ALL;
30
```

```

31  ENTITY KeyboardTB IS
32  END KeyboardTB;
33
34  ARCHITECTURE behavior OF KeyboardTB IS
35
36      -- Component Declaration for the Unit Under Test (UUT)
37
38      COMPONENT OctaveKeyboardTop
39      PORT(
40          keys : IN std_logic_vector(7 downto 0);
41          clk : IN std_logic;
42          led_disable : IN std_logic;
43          song_enable : IN std_logic;
44          tone : OUT std_logic;
45          shutdown : OUT std_logic;
46          key_out : OUT std_logic_vector(7 downto 0);
47          led_out : OUT std_logic_vector(7 downto 0)
48      );
49  END COMPONENT;
50
51
52      --Inputs
53      signal keys : std_logic_vector(7 downto 0) := (others => '0');
54      signal clk : std_logic := '0';
55      signal led_disable : std_logic := '0';
56      signal song_enable : std_logic := '0';
57
58      --Outputs
59      signal tone : std_logic;
60      signal shutdown : std_logic;
61      signal key_out : std_logic_vector(7 downto 0);

```

```

62      signal led_out : std_logic_vector(7 downto 0);
63
64      -- Clock period definitions
65      constant clk_period : time := 1 ns;
66
67      BEGIN
68
69          -- Instantiate the Unit Under Test (UUT)
70          uut: OctaveKeyboardTop PORT MAP (
71              keys => keys,
72              clk => clk,
73              led_disable => led_disable,
74              song_enable => song_enable,
75              tone => tone,
76              shutdown => shutdown,
77              key_out => key_out,
78              led_out => led_out
79          );
80
81          -- Clock process definitions
82          clk_process :process
83          begin
84              clk <= '0';
85              wait for clk_period/2;
86              clk <= '1';
87              wait for clk_period/2;
88          end process;
89
90
91          -- Stimulus process
92          stim_proc: process

```

```
93      begin
94          -- hold reset state for 100 ns.
95          wait for clk_period*10;
96
97          keys <= "10000000";
98          wait for clk_period*2;
99
100         wait;
101     end process;
102
103 END;
```

7.2.3 Resource utilization

Figure 13: Advanced HDL Synthesis Report

```

Macro Statistics
# Counters : 3
  14-bit up counter : 1
  32-bit up counter : 1
  4-bit up counter : 1
# Accumulators : 1
  13-bit up accumulator : 1
# Registers : 8
  Flip-Flops : 8
# Comparators : 2
  10-bit comparator greater : 1
  4-bit comparator equal : 1
# Multiplexers : 10
  1-bit 2-to-1 multiplexer : 2
  13-bit 2-to-1 multiplexer : 7
  8-bit 2-to-1 multiplexer : 1
# FSMs : 1

```

Figure 14: Device Utilization Summary

Slice Logic Utilization:

Number of Slice Registers:	189	out of	18224	1%
Number of Slice LUTs:	335	out of	9112	3%
Number used as Logic:	335	out of	9112	3%

Slice Logic Distribution:

Number of LUT Flip Flop pairs used:	346			
Number with an unused Flip Flop:	157	out of	346	45%
Number with an unused LUT:	11	out of	346	3%
Number of fully used LUT-FF pairs:	178	out of	346	51%
Number of unique control sets:	20			

IO Utilization:

Number of IOs:	29			
Number of bonded IOBs:	29	out of	232	12%
IOB Flip Flops/Latches:	2			

Specific Feature Utilization:

Number of BUFG/BUFGCTRLs:	2	out of	16	12%
---------------------------	---	--------	----	-----

7.2.4 UCF

Figure 15: UCF file

```

## Clock signal
NET "clk" LOC = "V10" | IOSTANDARD = "LVCMOS33";
Net "clk" TNM.NET = sys_clk_pin;
TIMESPEC TS_sys_clk_pin = PERIOD sys_clk_pin 100000 kHz;

## Leds
NET "led_out<0>" LOC = "U16" | IOSTANDARD = "LVCMOS33";
NET "led_out<1>" LOC = "V16" | IOSTANDARD = "LVCMOS33";
NET "led_out<2>" LOC = "U15" | IOSTANDARD = "LVCMOS33";
NET "led_out<3>" LOC = "V15" | IOSTANDARD = "LVCMOS33";
NET "led_out<4>" LOC = "M11" | IOSTANDARD = "LVCMOS33";
NET "led_out<5>" LOC = "N11" | IOSTANDARD = "LVCMOS33";
NET "led_out<6>" LOC = "R11" | IOSTANDARD = "LVCMOS33";
NET "led_out<7>" LOC = "T11" | IOSTANDARD = "LVCMOS33";

## Switches
NET "led_disable" LOC = "T10" | IOSTANDARD = "LVCMOS33";
NET "song_enable" LOC = "T9" | IOSTANDARD = "LVCMOS33";

##JA
NET "keys<4>" LOC = "T12" | IOSTANDARD = "LVCMOS33";
NET "keys<0>" LOC = "V12" | IOSTANDARD = "LVCMOS33";
NET "keys<5>" LOC = "N10" | IOSTANDARD = "LVCMOS33";
NET "keys<1>" LOC = "P11" | IOSTANDARD = "LVCMOS33";

##JB
NET "keys<6>" LOC = "K2" | IOSTANDARD = "LVCMOS33";
NET "keys<2>" LOC = "K1" | IOSTANDARD = "LVCMOS33";
NET "keys<7>" LOC = "L4" | IOSTANDARD = "LVCMOS33";
NET "keys<3>" LOC = "L3" | IOSTANDARD = "LVCMOS33";

##JD, LX16 Die only
NET "tone" LOC = "G11" | IOSTANDARD = "LVCMOS33";
NET "shutdown" LOC = "E11" | IOSTANDARD = "LVCMOS33";

```

7.3 Memory Map

7.4 Timing Diagram

The critical path is between clkcount_8 and clkcount_23 in kidsCounter. The delay is 4.866ns. Here is the excerpt from the synthesis report:

```
Timing constraint: Default period analysis for Clock 'clk_en'
Clock period: 4.866ns (frequency: 205.508MHz)
Total number of paths / destination ports: 3669 / 262
```

Delay: 4.866 ns (Levels of Logic = 3)
Source: kidsCounter/clkcount_8 (FF)
Destination: kidsCounter/clkcount_23 (FF)
Source Clock: clk_en rising
Destination Clock: clk_en rising

Data Path: kidsCounter/clkcount_8 to kidsCounter/clkcount_23

Cell : in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
FD:C->Q	3	0.525	1.221	kidsCounter/clkcount_8 (kidsCounter/clkcount_8)
LUT6:I0->O	7	0.254	1.186	
				kidsCounter/GND_11_o_clkcount [31]_equal_1_o <31>4
				(kidsCounter/GND_11_o_clkcount [31]_equal_1_o <31>3)
LUT5:I1->O	13	0.254	1.098	kidsCounter/_n00281 (kidsCounter/_n0028)
LUT4:I3->O	1	0.254	0.000	kidsCounter/clkcount_23_rstpot (kidsCounter/clkco
FD:D		0.074		kidsCounter/clkcount_23
Total		4.866 ns (1.361 ns logic , 3.505 ns route)		
				(28.0% logic , 72.0% route)

Based on this information, the maximum clock speed for this circuit is 205.508MHz, meaning the clock period must be at least 4.866ns.

7.5 Data Sheets

The proceeding pages contain data sheets for parts used in this project that are not already on the class website. They include data sheets for these parts:

- PmodAMP2
- PmodBB

PmodAMP2™ Reference Manual

Revision: August 2, 2012

Note: This document applies to REV B of the board.



1300 NE Henley Court, Suite 3

Pullman, WA 99163

(509) 334 6306 Voice | (509) 334 6300 Fax

Overview

The PmodAMP2 amplifies low power audio signals to drive a monophonic output. The module features a digital gain select that allows output at 6 dB and 12 dB with pop-and-click suppression. A Digilent 6-pin connector provides the audio input to the module and a 1/8-inch mono jack supplies the speaker output.

For customer convenience, Digilent has an inexpensive speaker and enclosure available for sale that is suitable for use with the PmodAMP2. Also, unlike most Digilent Pmod modules that accept only digital inputs, the PmodAMP2 accepts analog inputs and pulse width modulated digital inputs.

Inputs and Outputs (I/O)

The PmodAMP2 accepts either digital or analog inputs at a voltage range of 0-Vcc. Typically a Digilent system board supplies power to the module at 3.3V, though the maximum supply voltage is 5.0V. The connector J1 provides the audio input, gain select, shutdown select, and power. (See figure 1)

There are several suitable inputs for the PmodAMP2. The typical input is a pulse width modulated (PWM) signal produced by a digital output from a Digilent programmable logic system board or microcontroller board. The low pass filter on the input acts as a reconstruction filter to convert the PWM digital signal into an analog voltage on the amplifier input.


The PmodAMP2 also accepts analog inputs with an input voltage range of 0-Vcc. These inputs will often be from an analog to digital converter module, like the Digilent PmodDA1 or PmodDA2. The output of a digital to analog



Features Include:

- Analog Devices SSM2377: Filterless, High Efficiency, Mono 2.5 Watt Class-D Audio Amplifier
- Digital gain select
- Pop -and-click suppression
- Micropower shutdown mode
- 1/8-inch mono speaker jack
- A 6-pin header for input
- 2.5V – 5V operating voltage

Figure 1

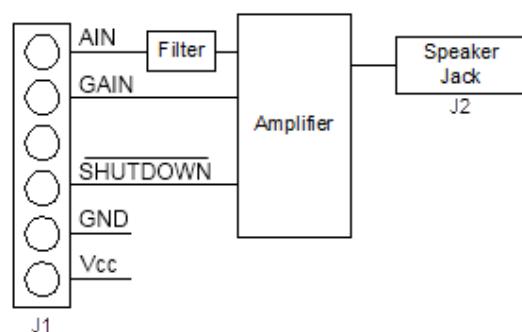

converter module will normally have a voltage range of 0-3.3V and should have a sample rate of at least 16Khz. The low pass filter on the input removes the high frequency artifacts generated during the sampling process.

Additionally, the PmodAMP2 accepts inputs from a variety of line level audio signals. A line level input, like the output of a portable CD player or MP3 player, will typically be a 1V peak-to-peak analog voltage. The input band-pass filter clarifies and amplifies the input voltage from the signal source and then directs the signal to the output jack to drive a speaker. The connector J2 operates as the speaker output. (See figure 1)

Functional Description

The gain on the PmodAMP2 may be selected by tying the GAIN input to either logic '1' or logic '0'. (See table 1)

Table 1

GAIN Input	Gain
1	6 decibels (dB)
0	12 decibels (dB)

The PmodAMP2 features a micropower shutdown mode with a typical shutdown current of 100 nA. Users can enable the shutdown by applying a logic low to the SHUTDOWN pin. A10K-ohm resistor pulls the pin down to ground. To operate the AMP2 users must ensure the SHUTDOWN pin is in the highest position.

Customers will generally use the PmodAMP2 module with a Digilent programmable logic system board or microcontroller board. These boards produce either a pulse width modulated digital signal or an analog signal via a digital to analog converter. Most Digilent system boards have 6-pin connectors that allow the PmodAMP2 to plug directly into the system board or to connect via a Digilent 6-pin cable.

Some older model Digilent boards may need a Digilent Module Interface Board (MIB) and a 6-pin cable to connect to the PmodAMP2. The MIB plugs into the system board and the cable connects the PmodAMP2 to the MIB.

Note: For more information about the operation and features of the Analog Devices SSM2377 Audio Amplifier integrated circuit please see the datasheet available at www.analog.com.

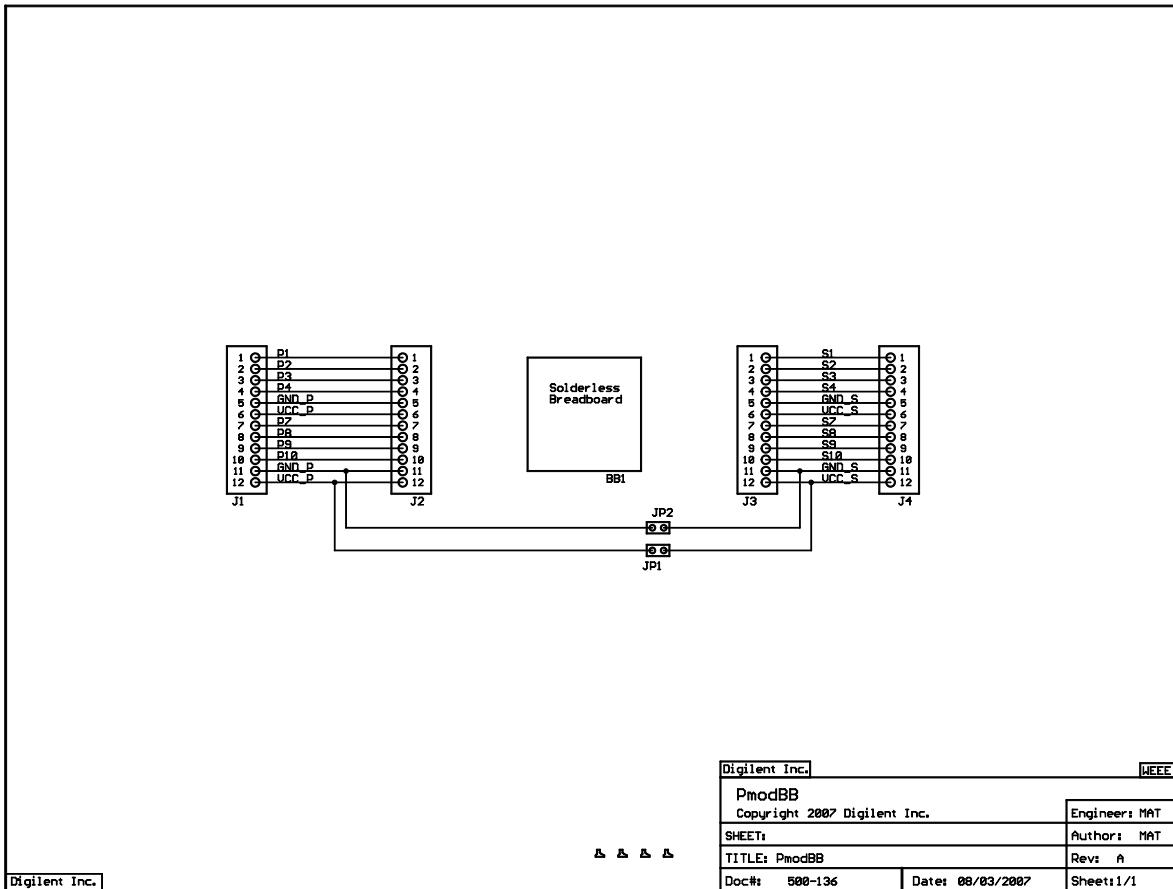


Figure 18: PmodBB Schematic